

Module 1 Hints: Boolean Logic

Hint #1

Remember ' is the NOT operator, + can be used as the OR operator, and * can be used as the AND operator.

Simplify the following expression:

$$AB + A'B + BC * A'C'$$

This is boolean algebra, so the same rules in arithmetic and algebra apply. So, we can re-write this as:

$AB + A'B + (A'C * BC')$ - we need both C and C' but this is impossible:

$AB + A'B$ - we factor out the B:

$B(A + A')$ - we use the complement law here, so $(A + A') = 1$:

$$B(1) = B \bullet$$

Simplify the following expression:

$$XY + XY' + X'Z + YZ$$

We can start by factoring out an X and a Z to get:


$$X(Y + Y') + Z(X' + Y)$$

We use the complement law to reduce $(Y + Y')$:

$$X(1) + Z(X' + Y) = X + Z(X' + Y) \bullet$$

Hint #2

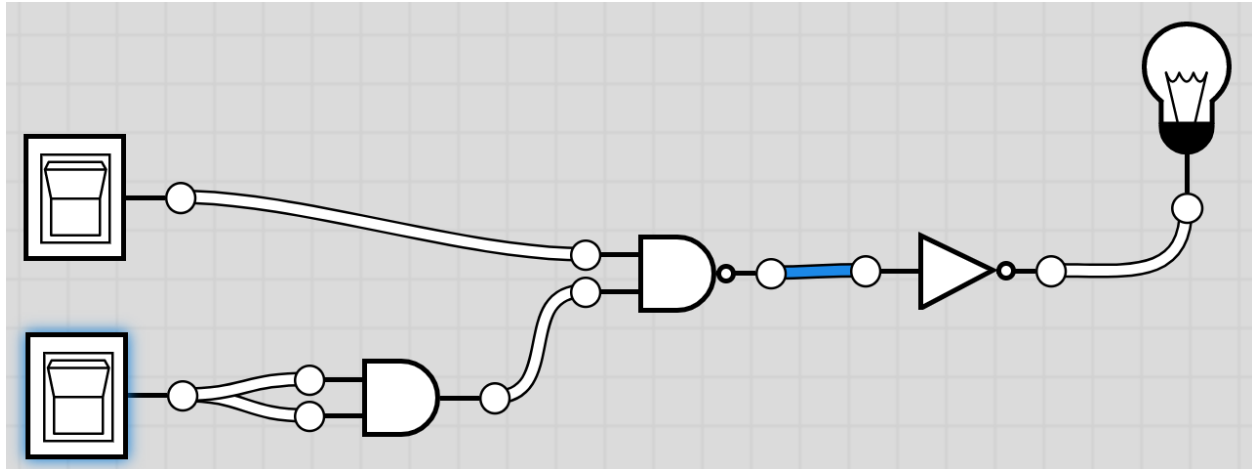For the following circuit, provide the simplified Boolean expression along with the corresponding truth table:



First we'll label the top switch (initially off) as X, and the bottom switch (initially off) as Y.

Notice Y comprises both inputs to the first AND gate. So, if Y is off both inputs are 0, and if Y is on, both inputs are a 1.

So, the first term in our expression, working from left to right, is **Y AND Y**

Next, we take the input from X and feed that into the NAND gate along with the output from the AND gate we discussed in the previous step. This gives us:

$$\mathbf{X \text{ NAND } (Y \text{ AND } Y)}$$

From the idempotent law, $(Y \text{ AND } Y) = Y$:

$$\mathbf{X \text{ NAND } Y}$$

Finally, we negate the entire output using the NOT gate before sending the output to the lightbulb:

$$\mathbf{\neg (X \text{ NAND } Y)}$$

The NOT negates the NAND and we're left with:

$$\mathbf{X \text{ AND } Y}$$

So, the lightbulb is on whenever X and Y are on at the same time. You can build and test it [here](#).

For a circuit with 2 inputs we have $2^2 = 4$ possible outputs. We know the lightbulb is off when X and Y are both true (1) and on otherwise, so our truth table becomes:

X	Y	Bulb
0	0	0
0	1	0

1	0	0
1	1	1