

JHU Computer Organization

Module 1 Assignment – Boolean/Digital Logic

Question #1: Boolean Operators

Given the following values for X, Y, and Z, are the following Boolean expressions true or false?

X = True, Y = True, Z = False

X	True
Y AND Y	True
(X NOR Z) AND Y	False
X XOR Y	False
(X XOR Z) AND (Y XOR Z)	True
(X OR X) XOR Z	True
(X NOR Z) XOR (Y OR Z)	True
(X NAND Z) OR Z	True
((NOT X AND NOT Y) AND Z) NAND X	True
(NOT X OR Y) NAND Z OR NOT Y XOR Z	True


Question #2: Simplifying Boolean Expressions

Simplify the given Boolean expression using the laws of Boolean logic. Show each simplification you make and please include the name of the law you used (e.g. complementation, idempotent, etc.) If you're having trouble getting started, remember this is just like Algebra. Collect like terms and factor them out of the logical expression the exact same way you would an algebraic equation. As a hint, although it isn't clear at first glance, the simplified expression contains just 2 terms!

$$X'YZ + XYZ + XY'Z' + XYZ' + XY'Z' + X'Y'Z' + WX'Y'Z' + W'X'Y'Z'$$

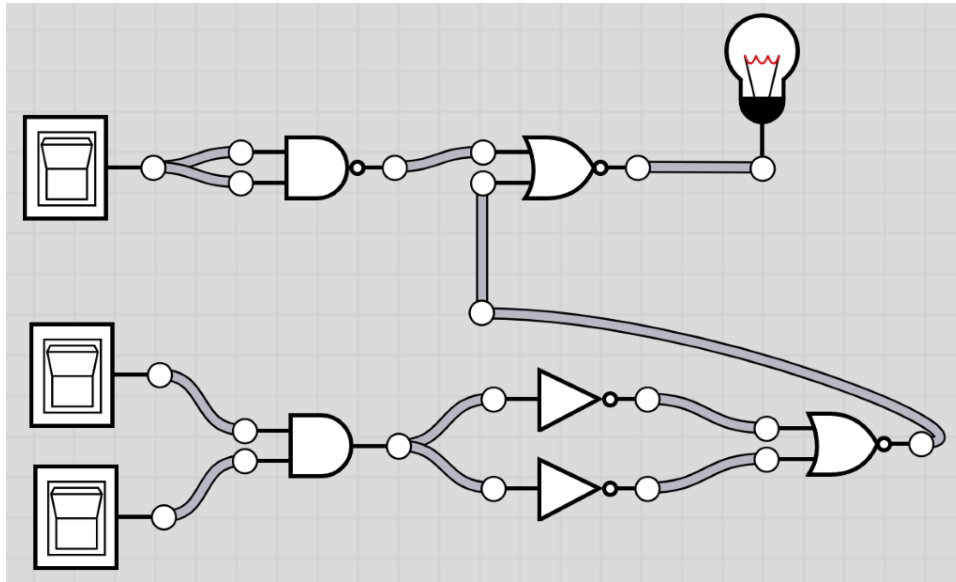Question #3: Digital Circuits & Truth Tables

Give both the simplified combinational Boolean expression and the truth table for the following circuit:



Simplified Boolean expression:

[illegible]

Question #4: Creating a Digital Circuit

Draw a circuit that implements the following Boolean logic expression and provide the corresponding truth table.

$$\neg(((W \wedge X) \otimes Y) \wedge Z)$$

[illegible]